

ECE 2040 HW 3

Saahas
Swaroop

Problem 4.2-2

Determine the node voltages for the circuit of Figure P 4.2-2.

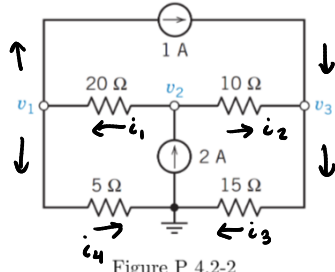


Figure P 4.2-2

$$\begin{aligned}
 i_3 + i_4 &= 2 & i_1 &= \frac{v_2 - v_1}{20} & \frac{v_2 - v_1}{20} + \frac{v_2 - v_3}{10} &= 2 \\
 i_2 + 1 &= i_3 & i_2 &= \frac{v_2 - v_3}{10} & v_2 - v_1 + 2v_2 - 2v_3 &= 40 \\
 i_1 + i_2 &= 2 & i_3 &= \frac{v_3}{15} & -v_1 + 3v_2 - 2v_3 &= 40 \\
 i_1 &= 1 + i_4 & i_4 &= \frac{v_1}{5} & \frac{v_2 - v_1}{20} &= 1 + \frac{v_1}{5} \\
 \frac{v_3}{15} + \frac{v_1}{5} &= 2 & & & v_2 - v_1 &= 20 + 4v_1 \\
 v_3 + 3v_1 &= 30 & & & -5v_1 + v_2 &= 20
 \end{aligned}$$

$$V = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} \begin{bmatrix} -1 & 3 & -2 \\ -5 & 1 & 0 \\ 0 & 3 & -5 \end{bmatrix} V = \begin{bmatrix} 40 \\ 20 \\ -30 \end{bmatrix}$$

$$\begin{aligned}
 \frac{v_2 - v_3}{10} + 1 &= \frac{v_3}{15} \\
 3v_2 - 3v_3 + 30 &= 2v_3 \\
 3v_2 - 5v_3 &= -30
 \end{aligned}$$

Problem 4.2-7

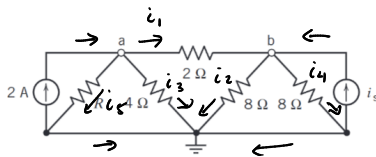
The node voltages in the circuit shown in Figure P 4.2-7 are $v_a = 7\text{ V}$ and $v_b = 10\text{ V}$. Determine values of the current source current, i_s , and the resistance, R .

Figure P 4.2-7

$$\begin{aligned}
 i_1 &= \frac{7 - 10}{2} = -1.5\text{ A} & i_s + i_1 &= i_2 + i_4 \\
 i_2 &= \frac{10}{8} = 1.25\text{ A} & i_s - 1.5 &= 2.5 \\
 i_3 &= \frac{7}{4} = 1.75\text{ A} & i_s &= \frac{7}{R} \\
 i_4 &= i_2 = 1.25\text{ A} & 1.75 &= \frac{7}{R} \\
 i_5 &= i_3 = 1.75\text{ A} & R &= 4\Omega
 \end{aligned}$$

Supernodes:

a & ground

c & d

$$\frac{v_b - v_a}{4\text{ k}\Omega} = i_1$$

$$\frac{v_d}{4\text{ k}\Omega} = i_2$$

$$v_c - v_d = 8$$

$$0 - v_a = 12$$

$$v_a = -12\text{ V}$$

$$i = 2\text{ mA} - i_1$$

$$i = 1\text{ mA} - i_2$$

 $\rightarrow$

$$2\text{ mA} - i_1 = 1\text{ mA} - i_2$$

$$1\text{ mA} = i_1 - i_2$$

$$\frac{v_b + 12}{4\text{ k}\Omega} - \frac{v_d}{4\text{ k}\Omega} = 1\text{ mA}$$

$$v_b + 12 - v_d = 4$$

$$v_b - v_d = -8$$

Problem 4.3-2

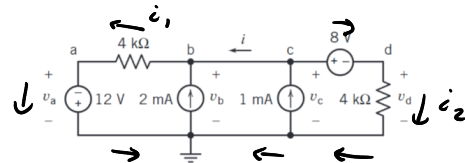
The voltages v_a , v_b , v_c , and v_d in Figure P 4.3-2 are the node voltages corresponding to nodes a, b, c, and d. The current i is the current in a short circuit connected between nodes b and c. Determine the values of v_a , v_b , v_c , v_d and of i .

Figure P 4.3-2

Problem 4.3-3

Determine the values of the power supplied by each of the sources in the circuit shown in Figure P 4.3-3.

Note: The voltages of the other nodes with unknown voltage can be expressed in terms of the node voltage v_a in Figure P 4.3-3.

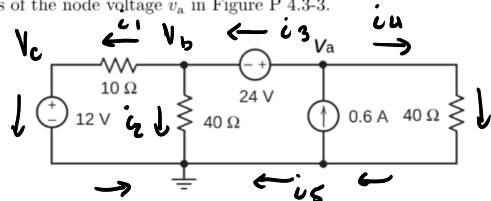


Figure P 4.3-3

$$V_a - V_b = 24$$

$$V_c = 12$$

$$\frac{V_b - V_c}{10} = i_1 \quad \frac{V_a}{40} = i_4$$

$$\frac{V_b}{40} = i_2$$

$$0.6 = i_1 + i_2 + i_4 \quad i_4 = i_5 + 0.6$$

$$i_1 + i_2 = i_3 \quad i_1 + i_2 + i_5 = 0$$